





## Summary of Circuits so far...

### - Combining resistors:

- Series   $\Rightarrow$    
 $R_{eq} = R_1 + R_2$

- Parallel

  $\Rightarrow$    
 $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$

### - Equations:

1. Ohm's law  $\rightarrow V = IR$



2. Power eqn.  $\rightarrow P = IV = I^2 R = \frac{V^2}{R}$

3. Energy eqn.  $\rightarrow E = Pt$

4. Kirchhoff's Voltage law  $\rightarrow$  voltage drops are equal to voltage gains


5. Kirchhoff's current law  $\rightarrow$  current into junction = current out junction
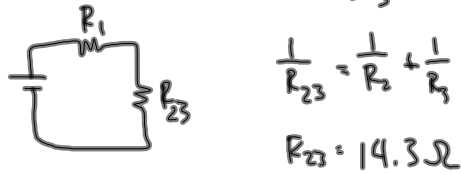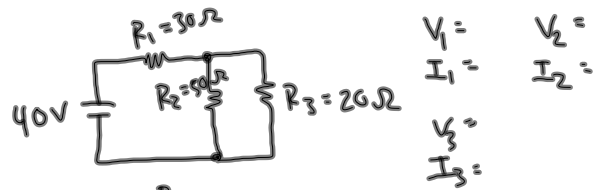
# Circuit Notes and Examples 1st Block 11.15.11



$$V_{total} = I_{total} R_{eq}$$
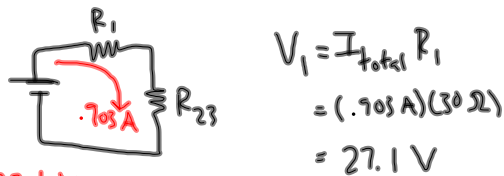
$$I_{total} = \frac{40V}{44.3 \Omega} = 0.903 A$$



$$V_1 = 27.1 V$$

$$I_1 = 0.903 A$$

$$V_{23} = I_{total} R_{23}$$

$$= (0.903 A)(14.3 \Omega)$$

$$= 12.9 V$$



$$V_2 = 12.9 V$$

$$I_2 = 0.258 A$$

$$V_{23} = I_2 R_2$$

$$I_2 = \frac{12.9 V}{50 \Omega}$$

$$= 0.258 A$$

$$V_3 = 12.9 V$$

$$I_3 = 0.645 A$$

$$V_{23} = I_3 R_3$$

$$I_3 = \frac{12.9 V}{20 \Omega}$$

$$= 0.645 A$$

$$P_{total} = I_{total} V_{total}$$


$$= (0.903 A)(40 V)$$

$$= 36.1 W$$

$$P_1 = I_1 V_1$$


$$P_2 = I_2 V_2$$

$$P_3 = I_3 V_3$$

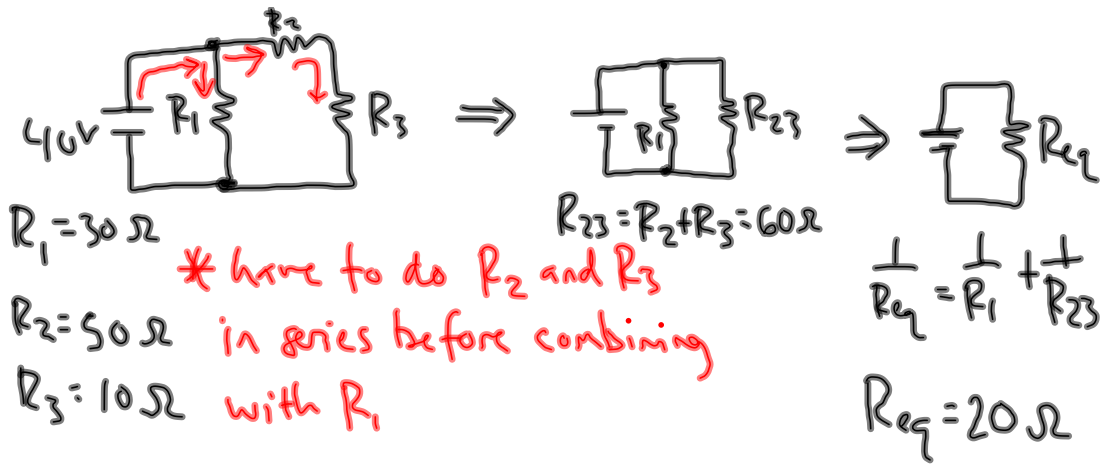


$$V_{total} = I_{total} R_{eq}$$
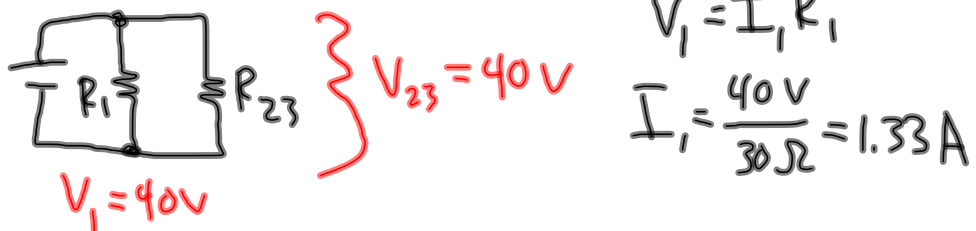
$$I_{total} = \frac{40V}{20\Omega} = 2A$$




$$V_{23} = I_{23} R_{23}$$
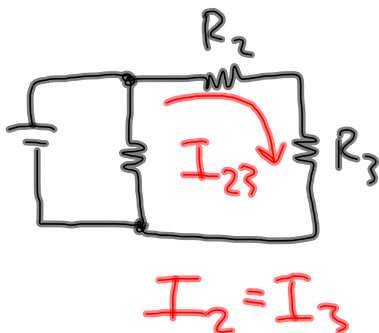
$$I_{23} = \frac{40V}{60\Omega} = .667A$$



$$\begin{aligned}
 V_2 &= I_2 R_2 \\
 &= (.667A)(50\Omega) \\
 &= 33.3V
 \end{aligned}$$

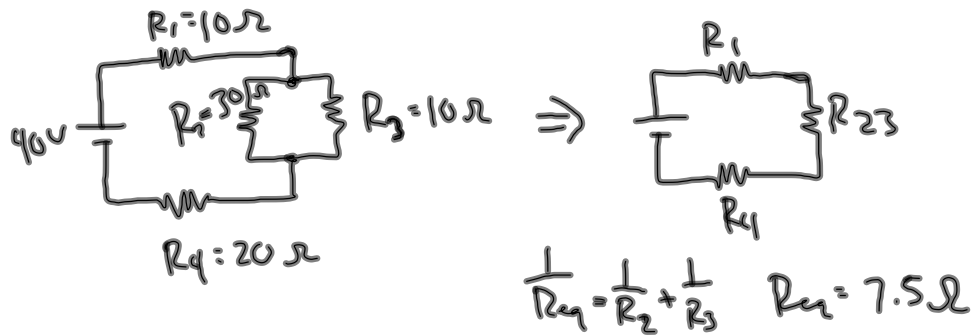
$$\begin{aligned}
 V_3 &= I_3 R_3 \\
 &= (.667A)(10\Omega) \\
 &= 6.67V
 \end{aligned}$$



$R_{eq}$   
 $R_{eq} = R_1 + R_{23} + R_4$   
 $= 37.5\Omega$

$$V_{total} = I_{total} R_{eq}$$

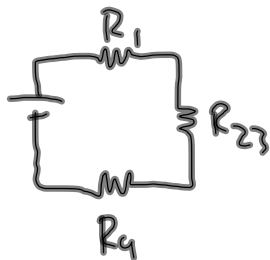
$$I_{total} = \frac{40V}{37.5\Omega} = 1.07A$$



$$\begin{aligned}
 V_1 &= I_{total} R_1 \\
 &= (1.07A)(10\Omega) \\
 &= 10.7V
 \end{aligned}$$

$$\begin{aligned}
 V_{23} &= I_{total} R_{23} \\
 &= (1.07A)(7.5\Omega) \\
 &= 8V
 \end{aligned}$$

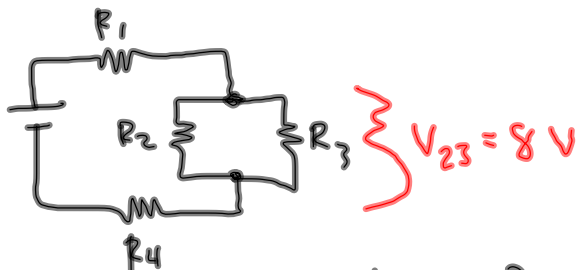
$$\begin{aligned}
 V_4 &= I_{total} R_4 \\
 &= (1.07A)(20\Omega) \\
 &= 21.3V
 \end{aligned}$$



$$\begin{aligned}
 V_{23} &= I_3 R_3 \\
 I_3 &= \frac{8V}{10\Omega} \\
 &= 0.8A
 \end{aligned}$$

$$\begin{aligned}
 V_{23} &= I_2 R_2 \\
 I_2 &= \frac{8V}{30\Omega} \\
 &= 0.26A
 \end{aligned}$$

Simplify this circuit:

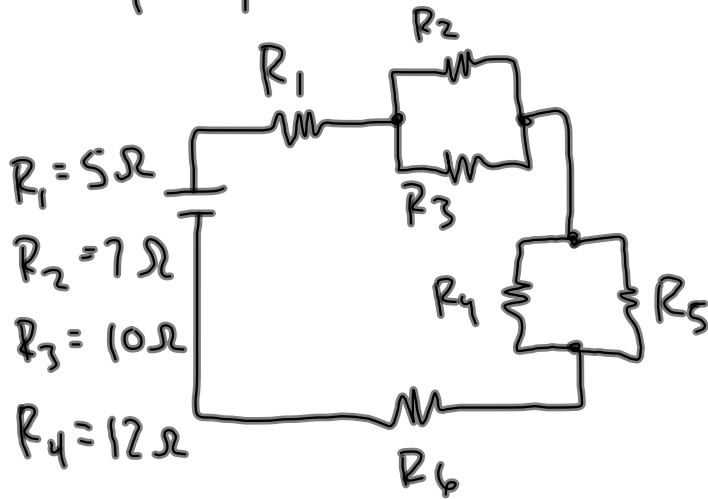

$$R_1 = 5\Omega$$


$$R_2 = 7\Omega$$

$$R_3 = 10\Omega$$

$$R_4 = 12\Omega$$


$$R_5 = 8\Omega$$

$$R_6 = 9\Omega$$

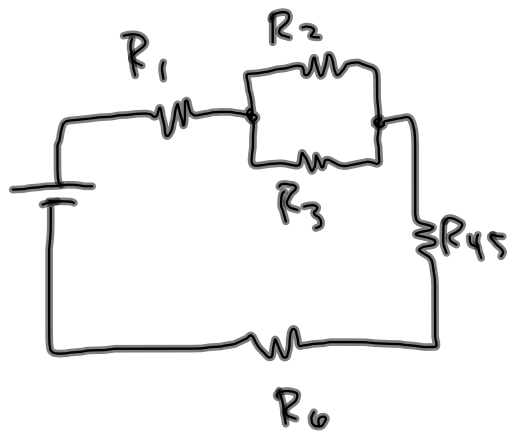


$$\frac{1}{R_{45}} = \frac{1}{R_4} + \frac{1}{R_5}$$

$$R_{45} = 4.8\Omega$$

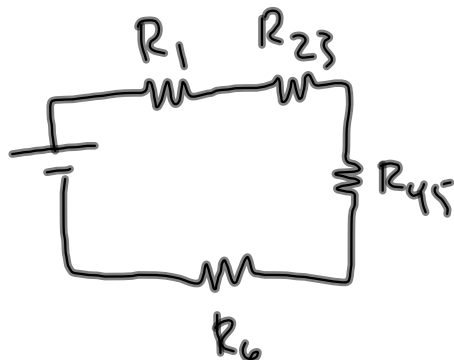

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{23} = 4.1\Omega$$

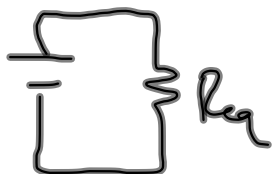

$$R_{eq} = R_1 + R_{23} + R_{45} + R_6$$

$$= 22.9\Omega$$